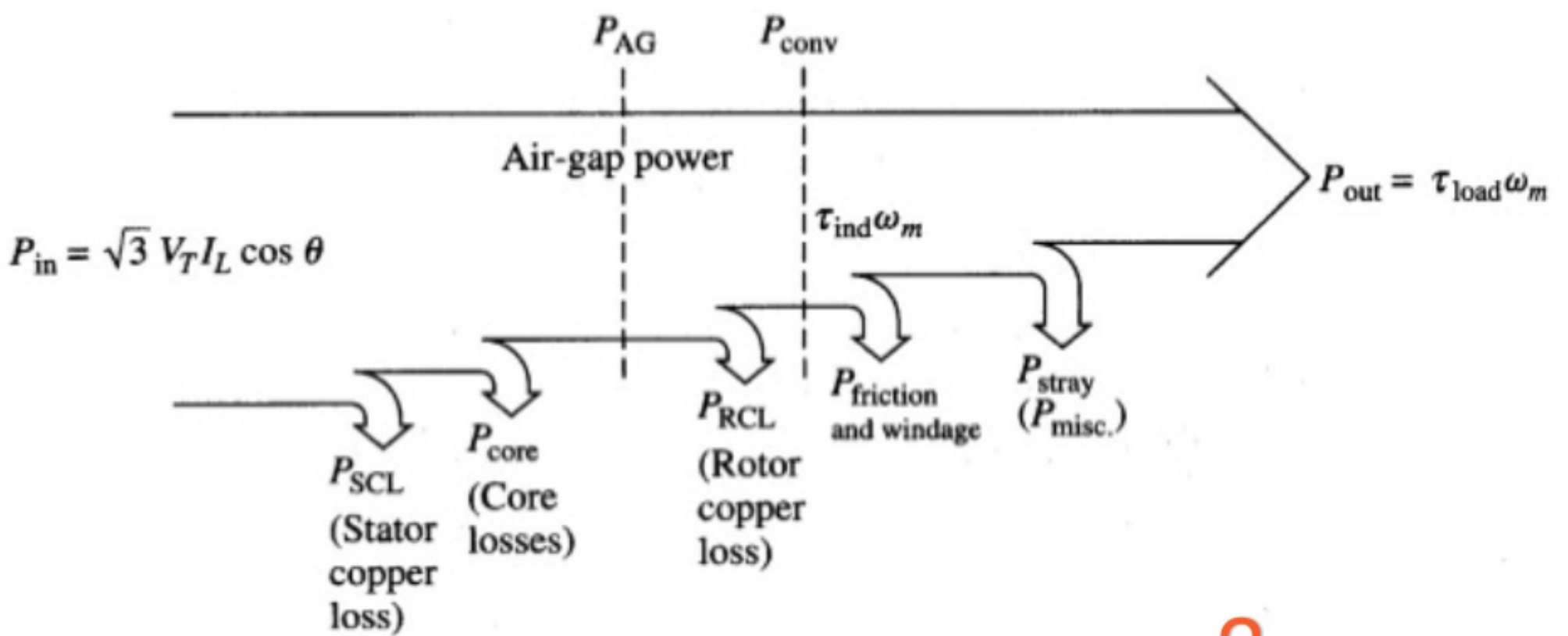


# Power losses in Induction machines

- Copper losses
  - Copper loss in the stator ( $P_{SCL} = I_1^2 R_1$ )
  - Copper loss in the rotor ( $P_{RCL} = I_2^2 R_2$ )
- Core loss ( $P_{core}$ )
- Mechanical power loss due to friction and windage
- How this power flow in the motor?

1

# Power flow in induction motor



2

## Power relations

$$P_{in} = \sqrt{3} V_L I_L \cos \theta = 3 V_{ph} I_{ph} \cos \theta$$

$$P_{SCL} = 3 I_1^2 R_1$$

$$P_{AG} = P_{in} - (P_{SCL} + P_{core})$$

$$P_{RCL} = 3 I_2^2 R_2$$

$$P_{conv} = P_{AG} - P_{RCL}$$


$$P_{out} = P_{conv} - (P_{f+w} + P_{stray})$$

$$\tau_{ind} = \frac{P_{conv}}{\omega_m}$$

3
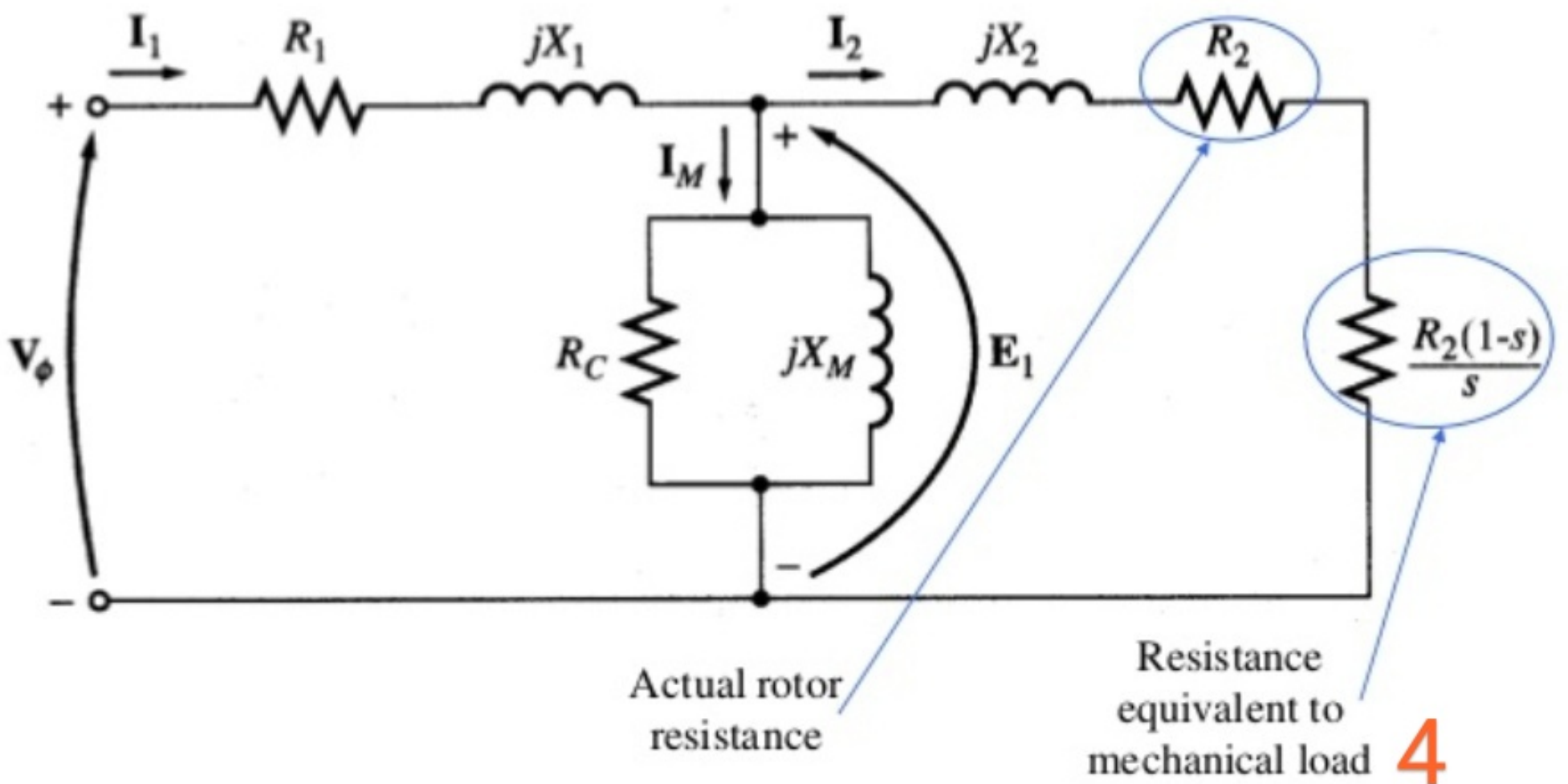
# Equivalent Circuit

- We can rearrange the equivalent circuit as follows



## Power relations

$$P_{in} = \sqrt{3} V_L I_L \cos \theta = 3 V_{ph} I_{ph} \cos \theta$$

$$P_{SCL} = 3 I_1^2 R_1$$

$$P_{AG} = P_{in} - (P_{SCL} + P_{core}) = P_{conv} + P_{RCL} = 3 I_2^2 \frac{R_2}{s} = \frac{P_{RCL}}{s}$$

$$P_{RCL} = 3 I_2^2 R_2$$


$$P_{conv} = P_{AG} - P_{RCL} = 3 I_2^2 \frac{R_2(1-s)}{s} = \frac{P_{RCL}(1-s)}{s}$$

$$P_{conv} = (1-s) P_{AG}$$

$$P_{out} = P_{conv} - (P_{f+w} + P_{stray}) \quad \tau_{ind} = \frac{P_{conv}}{\omega_m} = \frac{(1-s) P_{AG}}{(1-s) \omega_s}$$

5

# Power relations

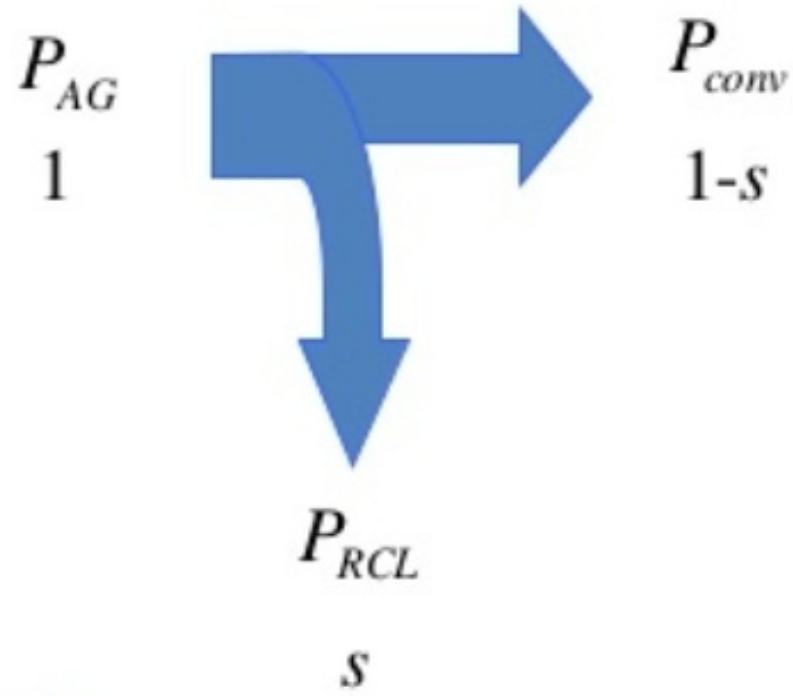

$P_{AG} : P_{RCL} : P_{conv}$
$1 : s : 1-s$

6