
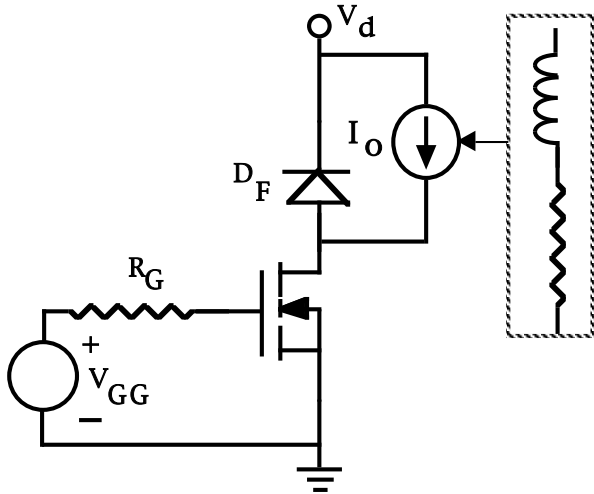


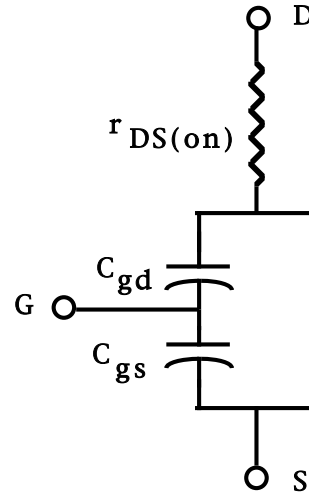
MOSFET Switching Models for Buck Converter



- Buck converter using power MOSFET.





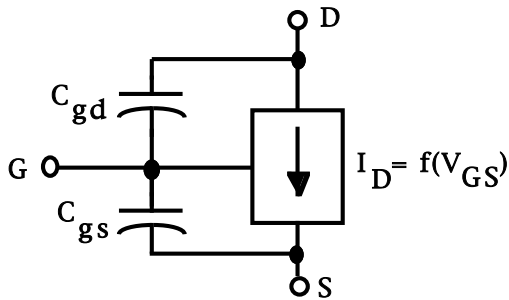- MOSFET equivalent circuit valid for on-state (triode) region operation.



- MOSFET equivalent circuit valid for off-state (cutoff) and active region operation.

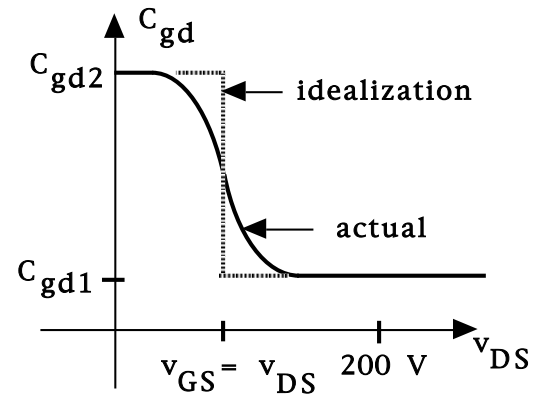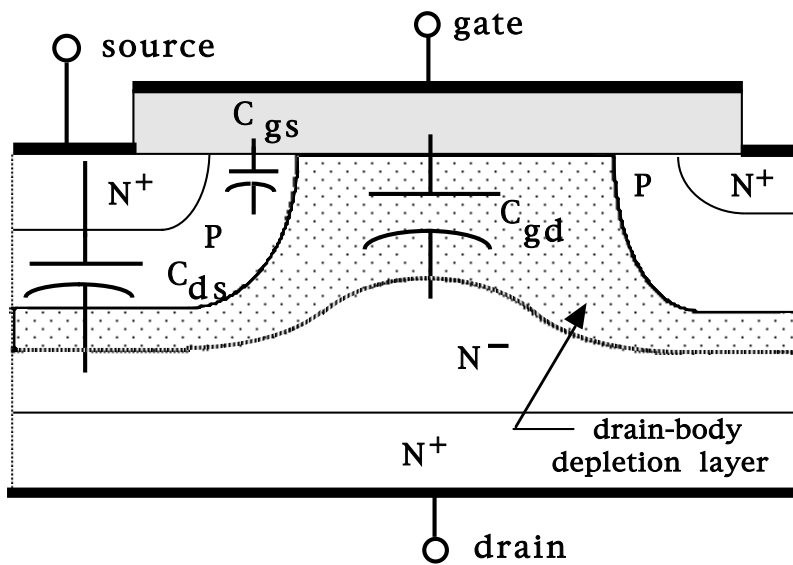
MOSFET Capacitances Determining Switching Speed




- Gate-source capacitance C_{gs} approximately constant and independent of applied voltages.
- Gate-drain capacitance C_{gd} varies with applied voltage. Variation due to growth of depletion layer thickness until inversion layer is formed.

Internal Capacitances Vs Spec Sheet Capacitances


MOSFET internal capacitances

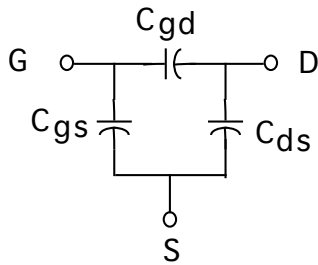

Input capacitance

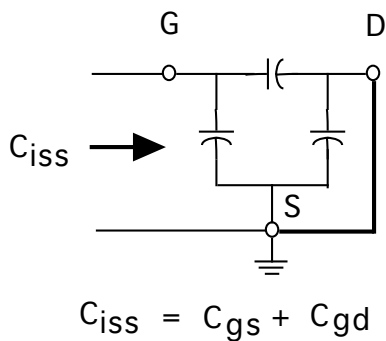


Reverse transfer or feedback capacitance

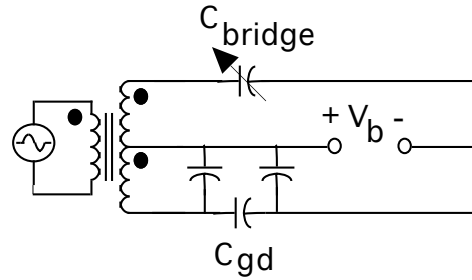


Bridge balanced ($V_b=0$) $C_{bridge} = C_{gd} = C_{rss}$

Output capacitance

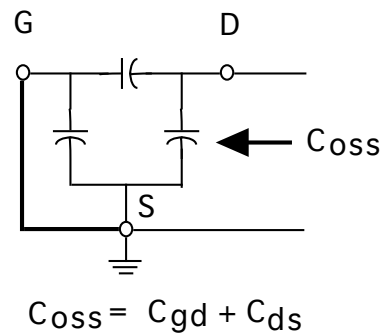


Turn-on Equivalent Circuits for MOSFET Buck Converter

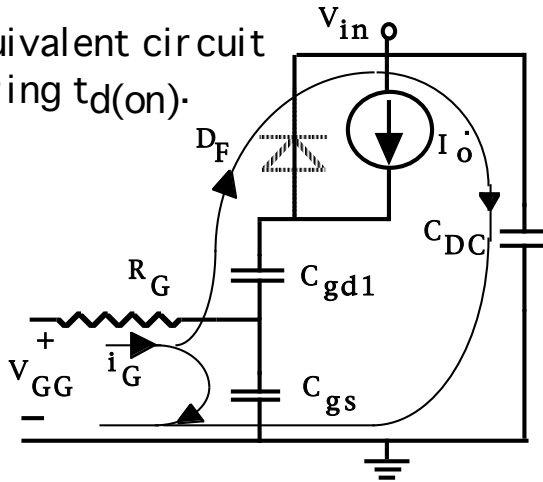
- Equivalent circuit during $t_d(\text{on})$.




- Equivalent circuit during t_{rj} .

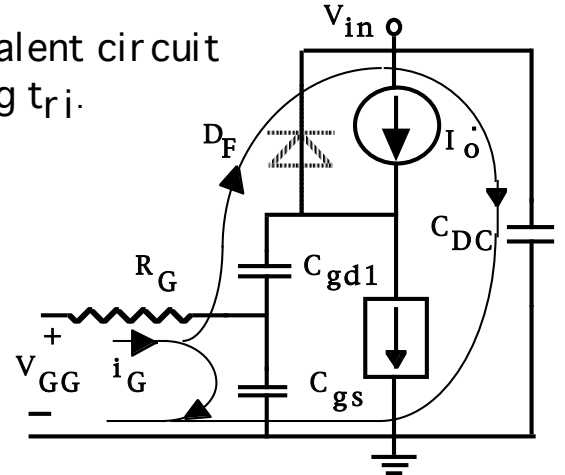


- Equivalent circuit during t_{fv1} .

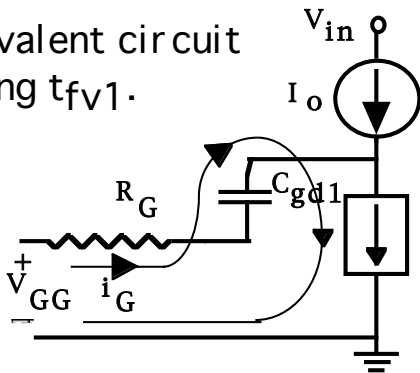

- Equivalent circuit during t_{fv2} .



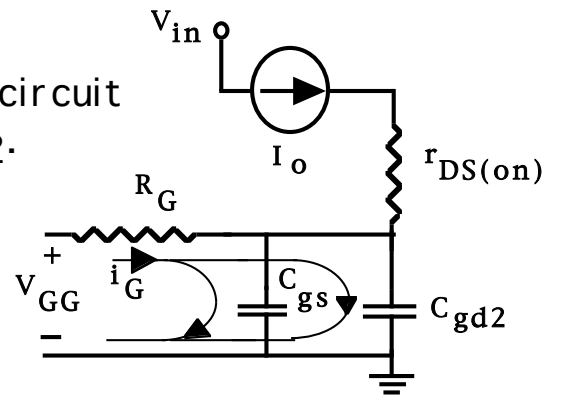


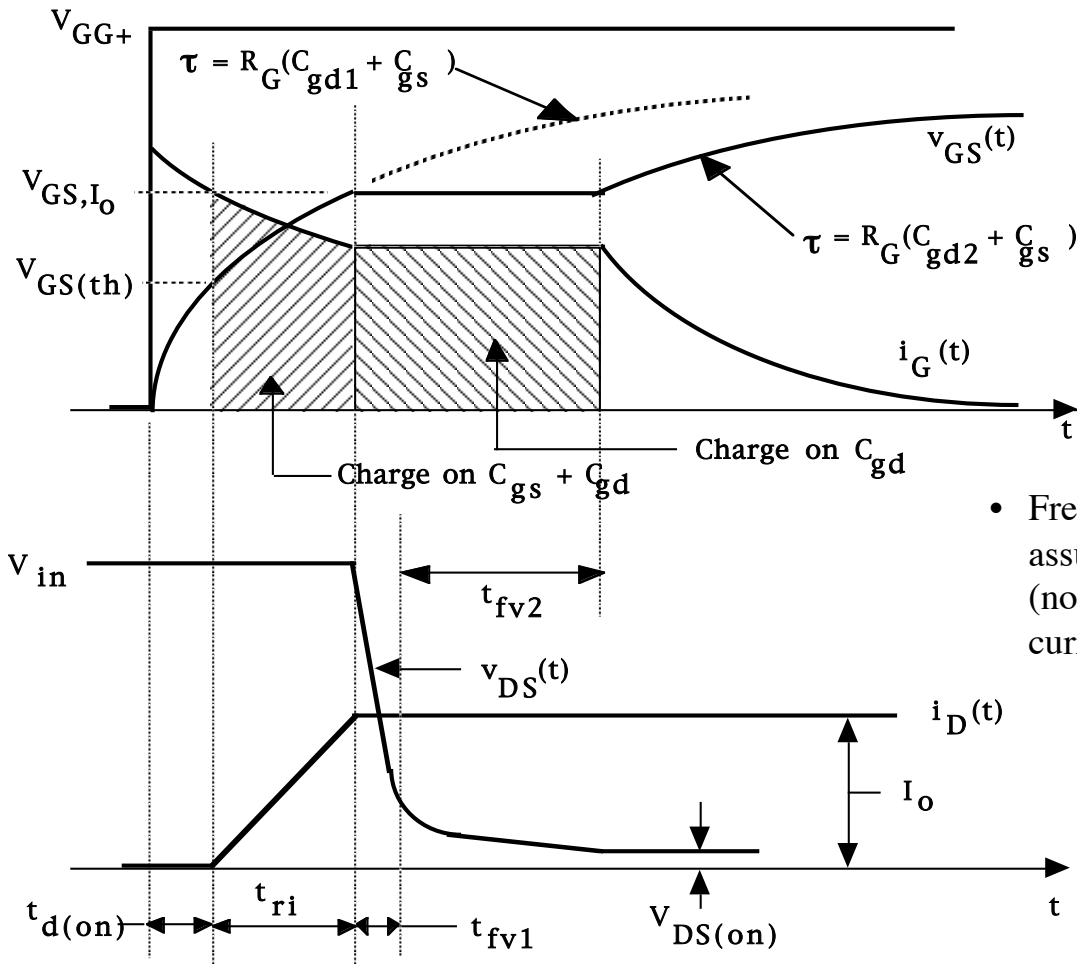MOSFET-based Buck Converter Turn-on Waveforms



- Free-wheeling diode assumed to be ideal. (no reverse recovery current).

Turn-on Gate Charge Characteristic

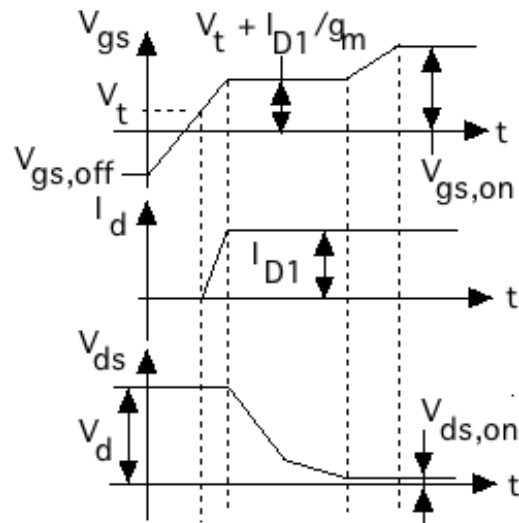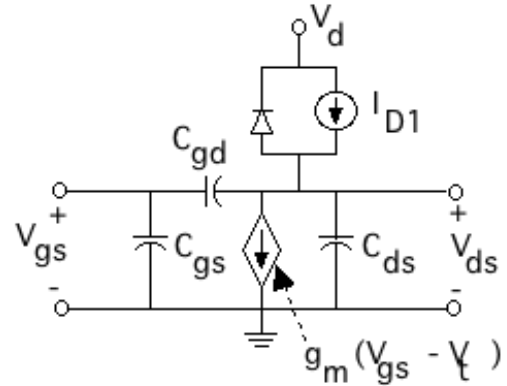
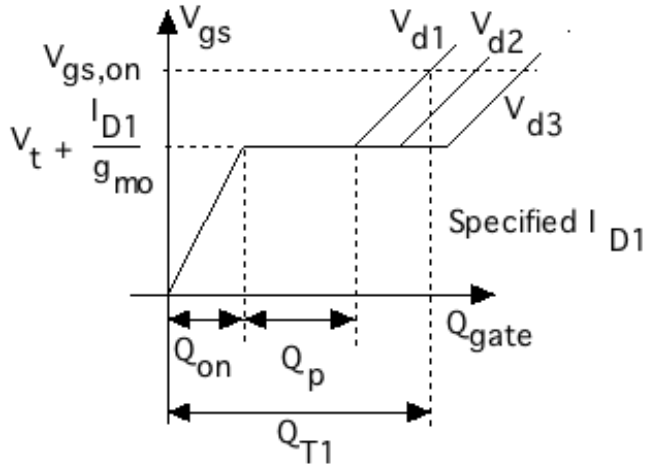


$$Q_{on} = \int_{V_{gs,off}}^{(V_t + I_{D1}/g_m)} [C_{gs}(V_{gs}) + C_{gd}(V_{gs})] V_{gs} dV_{gs}$$

$$Q_p = \int_{V_d}^{V_{ds,on}} C_{gd}(V_{ds}) V_{ds} dV_{ds}$$


$$Q_T = Q_{on} + Q_p + \int_{(V_t + I_{D1}/g_m)}^{V_{gs,on}} [C_{gs}(V_{gs}) + C_{gd}(V_{gs})] V_{gs} dV_{gs}$$

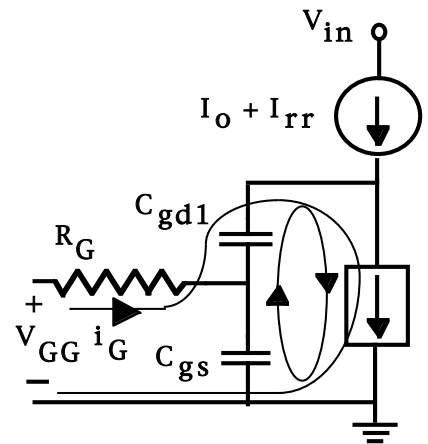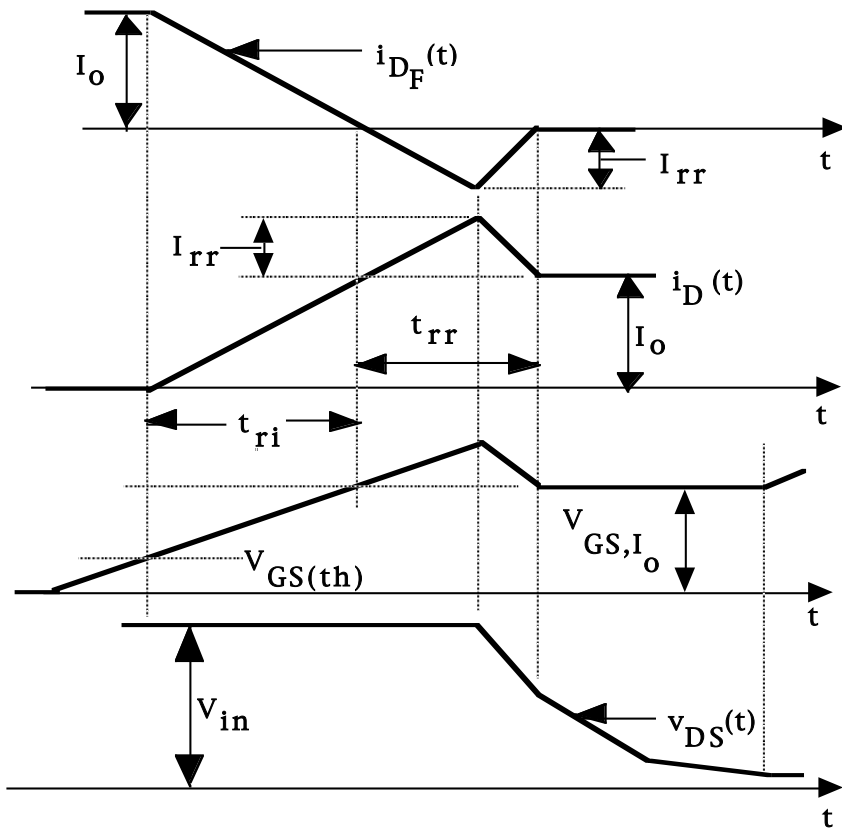Turn-on Waveforms with Non-ideal Free-wheeling Diode





- Equivalent circuit for estimating effect of free-wheeling diode reverse recovery.

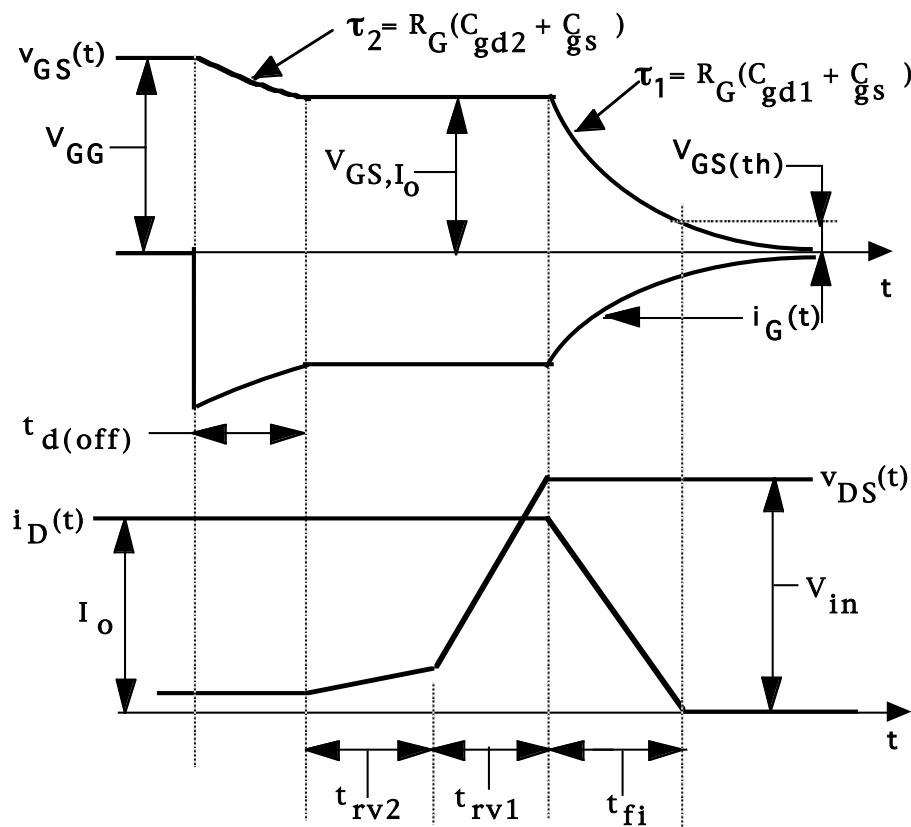MOSFET-based Buck Converter Turn-off Waveforms




- Assume ideal free-wheeling diode.
- Essentially the inverse of the turn-on process.
- Model quantitatively using the same equivalent circuits as for turn-on. Simply use correct driving voltages and initial conditions

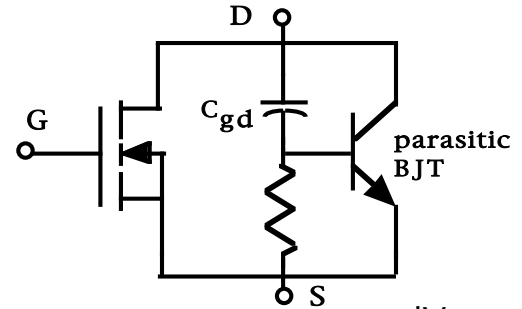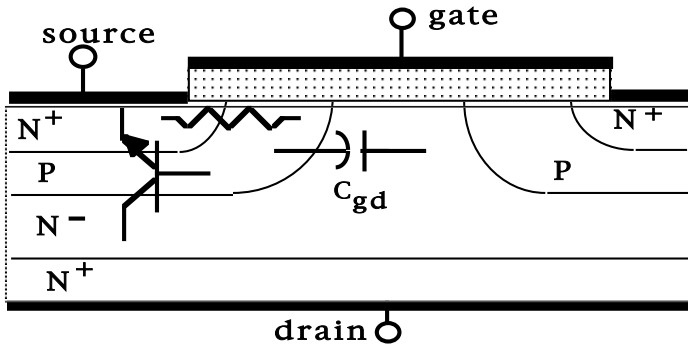dV/dt Limits to Prevent Parasitic BJT Turn-on



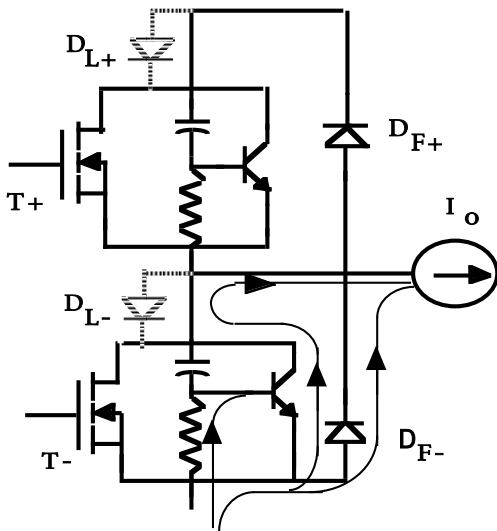- Large positive $C_{gd} \frac{dV_{DS}}{dt}$ could turn on parasitic BJT.



- Turn-on of T_+ and reverse recovery of D_{F-} will produce large positive $C_{gd} \frac{dv_{DS}}{dt}$ in bridge circuit.
- Parasitic BJT in T_- likely to have been in reverse active mode when D_{F-} was carrying current. Thus stored charge already in base which will increase likelihood of BJT turn-on when positive $C_{gd} \frac{dv_{DS}}{dt}$ is generated.

Maximum Gate-Source Voltage

- $V_{GS(max)}$ = maximum permissible gate-source voltage.
- If $V_{GS} > V_{GS(max)}$ rupture of gate oxide by large electric fields possible.
- $E_{BD(oxide)} \approx 5-10$ million V/cm
 - Gate oxide typically 1000 anstroms thick
 - $V_{GS(max)} < [5 \times 10^6] [10^{-5}] = 50$ V
 - Typical $V_{GS(max)}$ 20 - 30 V
- Static charge on gate conductor can rupture gate oxide
 - Handle MOSFETs with care (ground yourself before handling device)
 - Place anti-parallel connected Zener diodes between gate and source as a protective measure