Equivalent sequence networks

General sequence networks



Fig.3.1 (a)

Fig.3.1 (b)

2.4.1 SINGLE LINE TO GROUND FAULT

The termination of the three- phase access port as shown in fig. 3.2 brings about a condition of single line to ground fault through a fault impedance Z_f .

Typically Z_f is set to zero in all fault studies. I include Z_f in the analysis for the sake of generality. The terminal conditions at the fault point give the following equations:

- $I_b = 0$
- $I_c = 0$
- $V_a = I_a Z_f$





Connections of sequence networks for a single line to ground fault and its simplified equivalent circuit are shown in the fig. 3.3(a) and fig. 3.3 (b) below:

General sequence networks







Fig.3.3 (b)

Fig.3.3 (a)